


4:1 Multiplexer

Source Code And Output

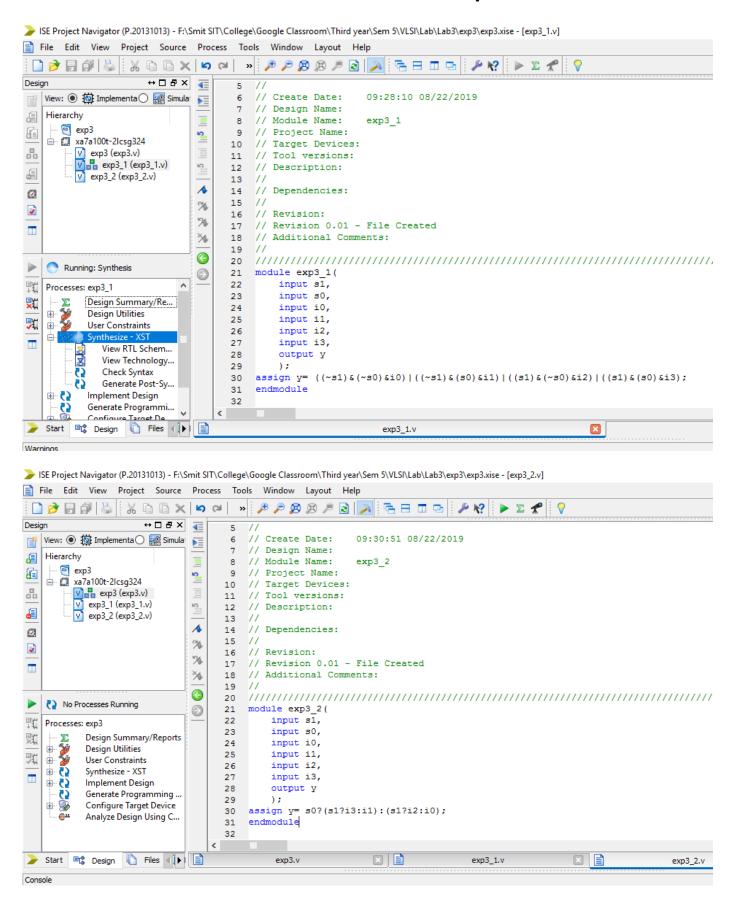


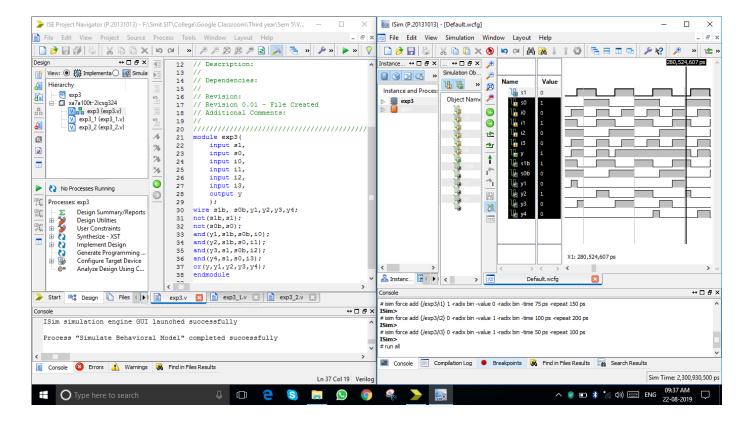


RTL Schematic with Gate Level Modelling

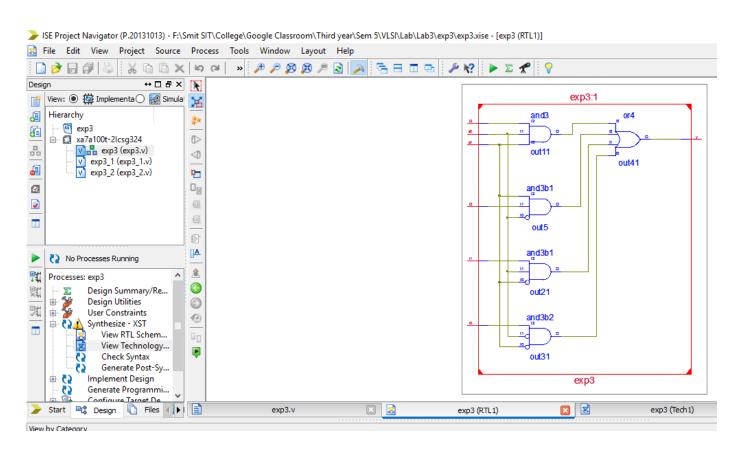

RTL Schematic with Data Flow Modelling

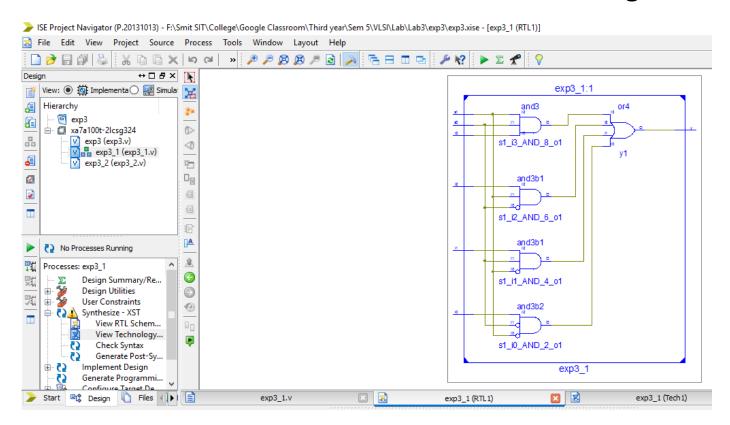

RTL Schematic with Assignment Operator

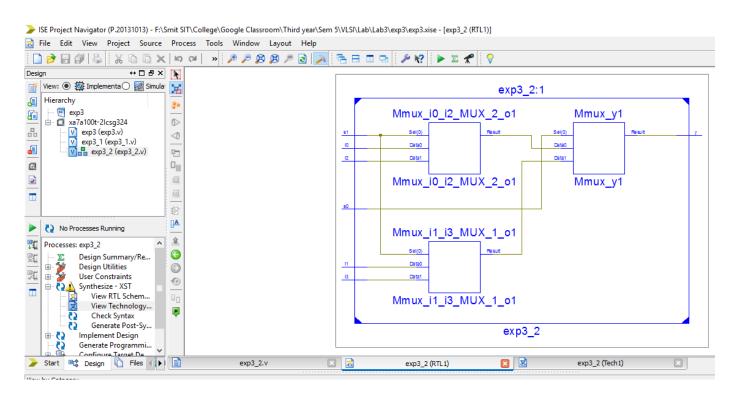

Technology Schematic

